

MODELLING OF FINITE STATE MACHINES

- Combinational and Sequential Circuits
 - In a combinational circuit, the outputs depend only on the applied input values and not on the past history.
 - In a sequential circuit, the outputs depend not only on the applied input values but also on the internal state.
 - The internal states also change with time.
 - The number of states is finite, and hence a sequential circuit is also referred to as a **Finite State Machine (FSM)**.
- Most of the practical circuits are sequential in nature.


Finite State Machine (FSM)

- A FSM can be represented either in the form of a ~~state table~~ state table or in the form of a state transition diagram.
 - Variations exist, eg. Algorithmic State Machine (ASM) chart.
- Example:
 - A circuit to detect 3 or more 1's in a serial bit stream.
 - The bits are applied serially in synchronism with a clock.
 - The outputs will become 1 whenever it detects 3 or more consecutive 1's in the stream.

STATE TABLE

Reset	PS	Input	NS	Output
1	-	-	A	0
0	A	0	A	0
0	A	1	B	0
0	B	0	A	0
0	B	1	C	0
0	C	0	A	0
0	C	1	D	1
0	D	0	A	0
0	D	1	D	1

STATE DIAGRAM

 



MEALY AND MOORE FSM TYPES

(2)

- A deterministic FSM can be mathematically defined as 5-tuple $(\Sigma, \Gamma, S, s_0, \delta, w)$ where Σ is the set of input combinations, Γ is the set of output combinations, S is a finite set of states, s_0 belongs to S , called as the initial state, δ is the ~~state-function~~ ^{state-transition} function, w is the output function.
- Here, $\delta: S \times \Sigma \rightarrow S$ \rightarrow cartesian product
- Present state (PS) and present input determines the next state (NS).
- For Mealy machine, $w: S \times \Sigma \rightarrow \Gamma$ (output depends on state + inputs)
- For Moore machine, $w: S \rightarrow \Gamma$ (output depends only on the state)

PICTORIAL DEPICTION



NS logic refers to the δ function

 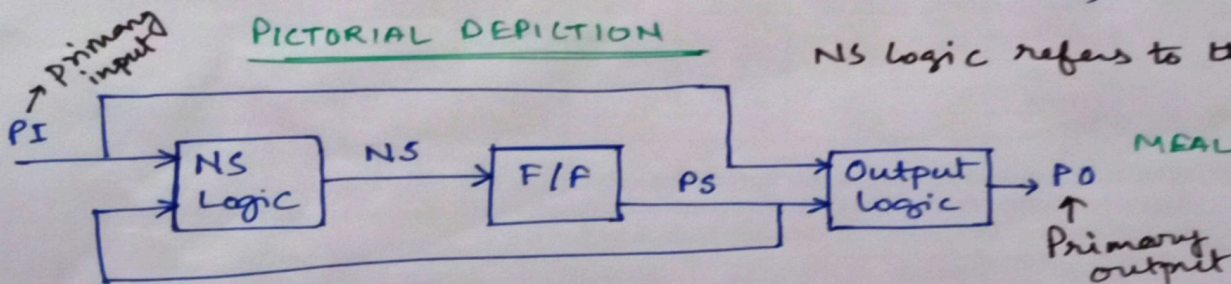

EXAMPLE-1

  (3)

- There are three lamps, RED, GREEN and YELLOW, that should glow cyclically with a fixed time interval (say, 1 second).
- Some observations:
 - The FSM will have three states, corresponding to the glowing state of the lamps.
 - The input set is null; state transition will occur whenever clock signal comes.
 - This is a Moore Machine, since the lamp that will glow only depends on the state and not on the inputs (here null).



module cyclic_lamp (clock, light);

input clock;

output reg [0:2] light;

parameter S0 = 0, S1 = 1, S2 = 2;

parameter RED = 3'b100, GREEN = 3'b010, YELLOW = 3'b001;

reg [0:1] state;

always @(posedge clock)

case (state)

S0: begin // S0 means RED

light ≤ GREEN;

state ≤ S1;

end

S1: begin // S1 means GREEN

light ≤ YELLOW;

state ≤ S2;

end

S2: begin

light ≤ RED;

state ≤ S0;


end

00 S0 → RED

01 S1 → GREEN

10 S2 → YELLOW

RGY

 


```
default: begin
    light ≤ RED;
    state ≤ S0;
end
endcase
endmodule
```

TestBench

```
module test_cyclic_lamp;
    reg clk;
    wire [0:2] light;
    cyclic_lamp LAMP (clock, light);
    always #5 clk = ~clk;
    initial
        begin
            clk = 1'b0;
            #100 $finish;
        end
    initial
        begin
            $dumpfile ("cyclic.vcd");
            $dumpvars(0, test_cyclic_lamp);
            $monitor ($time, "RGY: %b", light);
        end
endmodule
```

```
0   RGY: xxx
5   RGY: 100
15  RGY: 010
25  RGY: 001
35  RGY: 100
45  RGY: 010
55  RGY: 001
65  RGY: 100
75  RGY: 010
85  RGY: 001
95  RGY: 100
```

• Some comments on the solution:

- The synthesis tool will generate five flipflops - 2 for state, and 3 for light.
- The three output lines are also getting stored in flipflops.
 - We have used non-blocking assignment triggered by clock edge.
- But actually we do not need separate flipflops for the outputs, as the outputs can be directly generated from the state.
- How to achieve this?
 - Modify the Verilog code such that all assignments to light

is made in a separate "always" block.

- Use blocking assignment triggered by state change, and not by clock.

```
module cyclic_lamp (clock, light);
```

```
input clock;
```

```
output reg [0:2] light;
```

```
parameter S0=0, S1=1, S2=2;
```

```
parameter RED = 3'b100, GREEN = 3'b010, YELLOW = 3'b001;
```

```
reg [0:1] state;
```

```
always @(posedge clock)
```

```
case (state)
```

```
  S0: state <= S1;
```

```
  S1: state <= S2;
```

```
  S2: state <= S0;
```

```
  default: state <= S0;
```

```
endcase
```

```
always @(state)
```

```
case (state)
```

```
  S0: light = RED;
```

```
  S1: light = GREEN;
```

```
  S2: light = YELLOW;
```

```
  default: light = RED;
```

```
endcase
```

```
endmodule
```

- The synthesis tool will be generating only 2 flipflops corresponding to the first clock-triggered "always" block.

- The second "always" block will be generating a combinational circuit that takes state as input and produces light as the outputs.

State		Light		
S ₁	S ₀	R	G	Y
0	0	1	0	0
0	1	0	1	0
1	0	0	0	1
1	1	X	X	X

Logic expression after minimization is:

$$R = \bar{S}_0 \cdot \bar{S}_1$$



$$G = S_0$$

$$Y = S_1$$

  Example - 2

• Design of a serial parity detector.

- A continuous stream of bits is fed to a circuit in synchronous with a clock. The circuit will be generating a bit stream as output, where a 0 will indicate "even number of 1's seen so far" and a 1 will indicate "odd number of 1's seen so far".
- Also a Moore Machine



```


module parity_gen (x, clk, z);
    input x, clk;
    output reg z;
    reg even-odd; // The machine state
    parameter EVEN = 0, ODD = 1;


    always @(posedge clk)
        case (even-odd)
            EVEN: begin
                z <= x ? 1 : 0;
                even-odd <= x ? ODD : EVEN;
            end
            ODD: begin
                z <= x ? 0 : 1;
                even-odd <= x ? EVEN : ODD;
            end
            default: even-odd <= EVEN;
        end case
endmodule
    
```

This design will cause the synthesizer tool to generate a latch for the output "even-odd".

Testbench

```
module test_parity;  
  reg clk, x;  
  wire z;  
  parity_gen PAR(x, clk, z);  
  initial  
    begin  
      $dumpfile("parity.vcd"); $dumpvars(0, test_parity);  
      clk = 1'b0;  
    end  
  always #5 clk = ~clk;  
  initial  
    begin  
      #2 x = 0; #10 x = 1; #10 x = 1; #10 x = 1;  
      #10 x = 0; #10 x = 1; #10 x = 1; #10 x = 0;  
      #10 x = 0; #10 x = 1; #10 x = 1; #10 x = 0;  
      #10 $finish;  
    end  
end  
endmodule
```

 

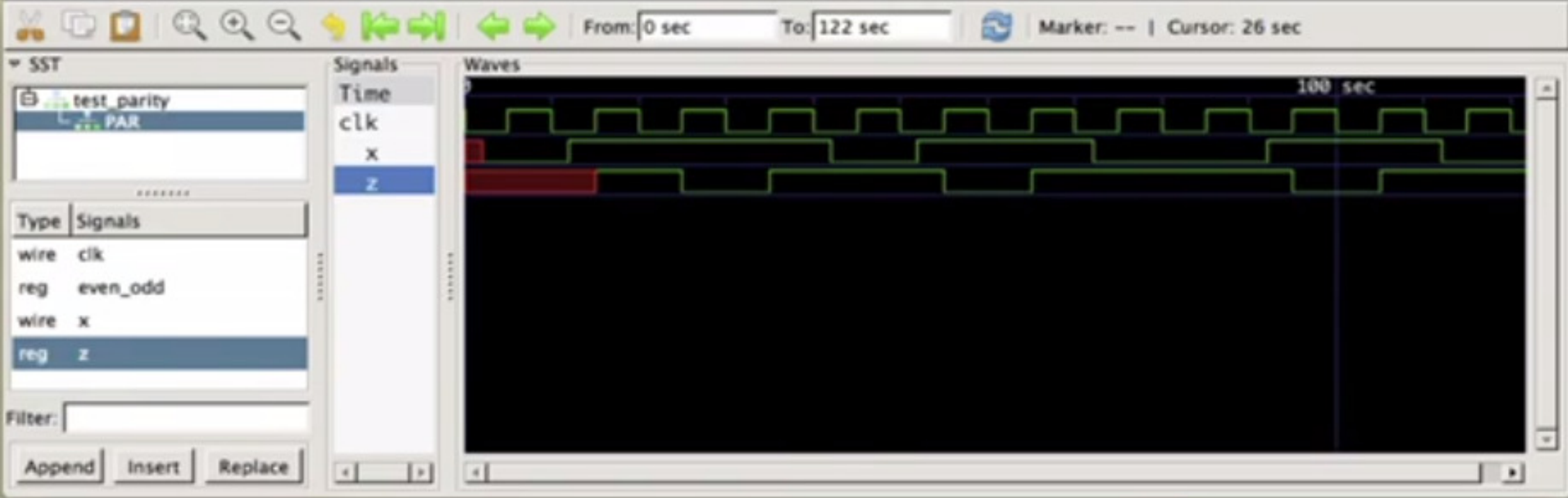


• Design of a sequence detector

- A circuit accepts a serial bit stream "x" as input and produces a serial bit stream "z" as output.
- Whenever the bit pattern "0110" appears in the input stream, it outputs $z = 1$; at all other times, $z = 0$.
- Overlapping occurrences of the pattern are also detected.
- This is a Mealy machine


x: 0 1 1 0 1 1 0

z: 0 0 0 1 0 0 1

 - Example: $x \rightarrow 0 \ 1 \ 0 \ 1 \ 0 \ 1 \ 1 \ 0 \ 1 \ 1 \ 0 \ 0 \ 1 \ 0 \ 1 \ 1 \ 0$
 $z \rightarrow 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 1 \ 0 \ 0 \ 1 \ 0 \ 0 \ 0 \ 0 \ 0 \ 1 \ 0 \ 0 \ 0 \ 0$



 The inputs bits "x" are applied in synchronism with the clock.



Sequence detector for pattern "0110"

(9)

```
module seq-detector (x, clk, reset, z);
  input x, clk, reset;
  output reg z;
  parameter s0 = 0, s1 = 1, s2 = 2, s3 = 3;
  reg [0:1] PS, NS;
```

```
always @(posedge clk or posedge reset)
```

```
  if (reset)
```

```
    PS ≤ s0;
```

```
  else
```

```
    PS ≤ NS;
```

```
  always @(PS, x)
```

```
    case (PS)
```

```
      s0: begin
```

```
        z = x ? 0 : 0;
```

```
        NS = x ? s0 : s1;
```

```
      end
```

```
      s1: begin
```

```
        z = x ? 0 : 0;
```

```
        NS = x ? s2 : s1;
```

```
      end
```

```
      s2: begin
```

```
        z = x ? 0 : 0;
```

```
        NS = x ? s3 : s1;
```

```
      end
```

```
      s3: begin
```


```
        z = x ? 0 : 1;
```

```
        NS = x ? s0 : s1;
```

```
      end
```

```
    endcase
```

```
endmodule
```

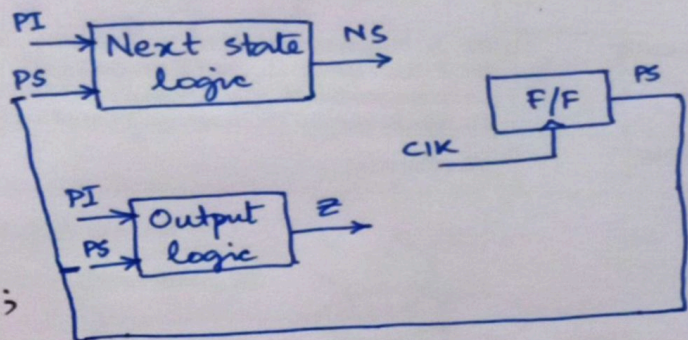

Test bench

```
module test-sequence;
  reg clk, x, reset; wire z;
  seq-detector SEQ (x, clk, reset, z);
  initial
```

```
  begin
```

```
    $dumpfile("sequence.vcd");
```

```
    $dumpvars(0, test-sequence);
```

```
    clk = 1'b0; reset = 1'b1;
```

```
    #15 reset = 1'b0;
```

```
  end
```

```
  always #5 clk = ~clk;
```

```
  initial
  begin
```

```
    #12 x=0; #10 x=0; #10 x=1; #10 x=1;
```

```
    #10 x=0; #10 x=1; #10 x=1; #10 x=0;
```

```
    #10 x=0; #10 x=1; #10 x=1; #10 x=0;
```

```
    #10 $finish;
```

```
  end
```

```
endmodule
```


SST

test_sequence

Type	Signals
reg	NS[0:1]
reg	PS[0:1]
wire	clk
wire	reset
wire	x
reg	z

Filter:

Append Insert Replace

Signals

Time

clk

reset

x

z

Waves



Example 4 (Homework)


- Design a sequence detector for the bit pattern "101010".
 - Work out the state diagram in a similar way.
 - Then code the state diagram in Verilog.

Serial Adder:

$$\begin{array}{r}
 A: 0110 \\
 B: 0010 \\
 \hline
 S: 01000
 \end{array}$$

State: CARRY
(1 bit)
 
$$\begin{array}{r}
 0 \\
 1 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 0 \\
 \hline
 1
 \end{array}$$



$$\begin{array}{r}
 1 \\
 0 \\
 \hline
 0
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 1 \\
 \hline
 1
 \end{array}$$

