

## DataPath & ControlPath Design Methodologies

**Dr. PRITAM BHATTACHARJEE**

*Assistant Professor (Senior Grade 2), Senior Member IEEE*

**School of Electronics Engineering (SENSE)**

**Vellore Institute of Technology – Chennai**

*pritam.bhattacharjee@vit.ac.in, +91 8132863424*



## Introduction

- In a complex digital system, the hardware is typically partitioned into two parts:
  - a) *Data Path*, which consists of the functional units where all computations are carried out.
    - Typically consists of registers, multiplexers, bus, adders, multipliers, counters, and other functional blocks.
  - b) *Control Path*, which implements a finite-state machine and provides control signals to the data path in proper sequence.
    - In response to the control signals, various operations are carried out by the data path.
    - Also takes inputs from the data path regarding various status information.

reg [15:0] A, B, C, D;


$$A = B + C$$

$$D = A - C$$

  

 
## Example 1: Multiplication by Repeated Addition


- We consider a simple algorithm using repeated addition.
  - Assume B is non-zero.



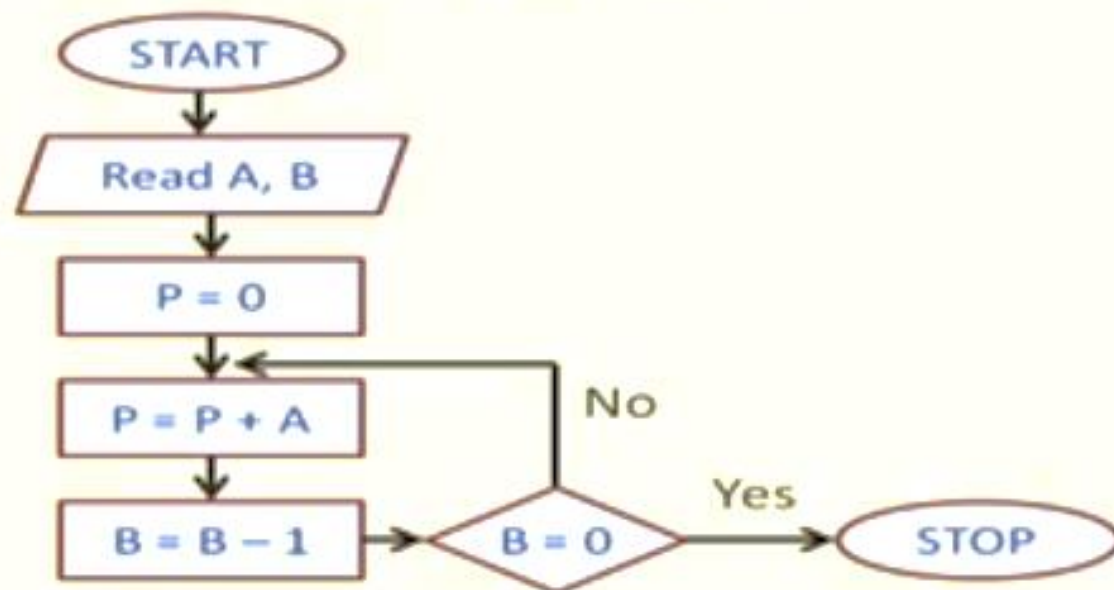
## Example 1: Multiplication by Repeated Addition

- We consider a simple algorithm using repeated addition.
  - Assume  $B$  is non-zero.
- We identify the functional blocks required in the data path, and the corresponding control signals.
- Then we design the FSM to implement the multiplication algorithm using the data path.





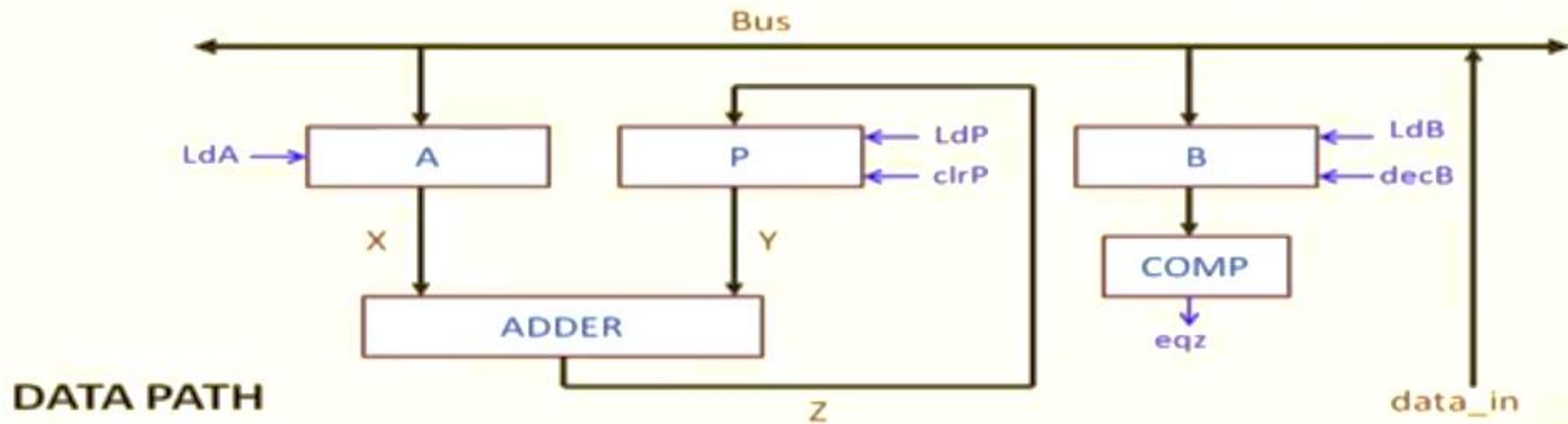

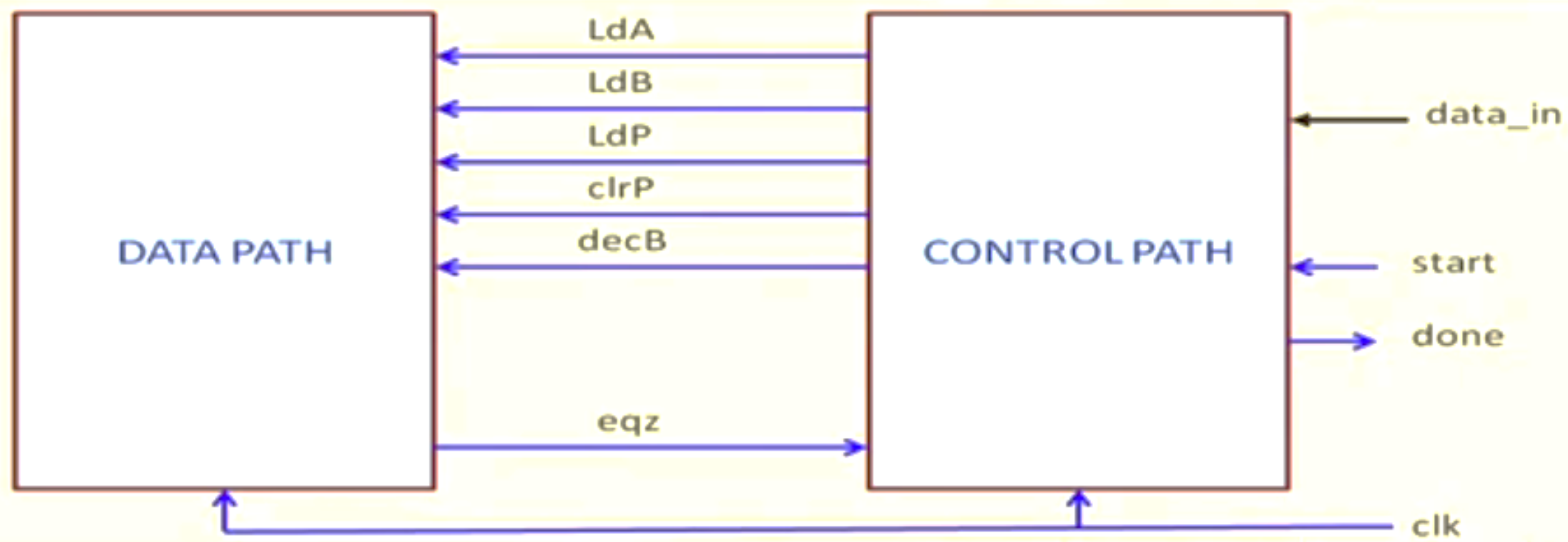



# CONTROL PATH

  



```
module MUL_datapath (eqz, LdA, LdB, LdP, clrP, decB, data_in, clk);  
  input LdA, LdB, LdP, clrP, decB, clk;  
  input [15:0] data_in;  
  output eqz;  
  wire [15:0] X, Y, Z, Bout, Bus;  
  
  PIP01 A (X, Bus, LdA, clk);  
  PIP02 P (Y, Z, LdP, clrP, clk);  
  CNTR B (Bout, Bus, LdB, decB, clk);  
  ADD AD (Z, X, Y);  
  EQZ COMP (eqz, Bout);  
endmodule
```

**THE DATA  
PATH**

```

module PIP01 (dout, din, ld, clk);
    input [15:0] din;
    input ld, clk;
    output reg [15:0] dout;
    always @(posedge clk)
        if (ld) dout <= din;
endmodule

```

```

module ADD (out, in1, in2);
    input [15:0] in1, in2;
    output reg [15:0] out;
    always @(*)
        out = in1 + in2;
endmodule

```

```

module PIP02 (dout, din, ld,
              clr, clk);
    input [15:0] din;
    input ld, clr, clk;
    output reg [15:0] dout;
    always @(posedge clk)
        if (clr) dout <= 16'b0;
        else if (ld) dout <= din;
endmodule

```

```

module EQZ (eqz, data);
    input [15:0] data;
    output eqz;
    assign eqz = (data == 0);
endmodule

```

```
module CNTR (dout, din, ld, dec, clk);  
    input [15:0] din;  
    input ld, dec, clk;  
    output reg [15:0] dout;  
    always @(posedge clk)  
        if (ld) dout <= din;  
        else if (dec) dout <= dout - 1;  
endmodule
```

```
module controller (LdA, LdB, LdP, clrP, decB, done, clk, eqz, start);
  input clk, eqz, start;
  output reg LdA, LdB, LdP, clrP, decB, done;

  reg [2:0] state;
  parameter S0=3'b000, S1=3'b001, S2=3'b010, S3=3'b011, S4=3'b100;

  always @(posedge clk)
    begin
      case (state)
        S0:    if (start) state <= S1;
        S1:    state <= S2;
        S2:    state <= S3;
        S3:    #2 if (eqz) state <= S4;
        S4:    state <= S4;
        default: state <= S0;
      endcase
    end
end
```

**THE CONTROL  
PATH**

```
always @(state)
begin
    case (state)
        S0:    begin #1 LdA = 0;  LdB = 0; LdP = 0; clrP = 0; decB = 0; end
        S1:    begin #1 LdA = 1; end
        S2:    begin #1 LdA = 0; LdB = 1; clrP = 1; end
        S3:    begin #1 LdB = 0; LdP = 1; clrP = 0; decB = 1; end
        S4:    begin #1 done = 1; LdB = 0; LdP = 0; decB = 0; end
        default: begin #1 LdA = 0; LdB = 0; LdP = 0; clrP = 0; decB = 0; end
    endcase
end
endmodule
```

## THE TEST BENCH

```
module MUL_test;  
  reg [15:0] data_in;  
  reg clk, start;  
  wire done;
```

```
MUL_datapath DP (eqz, LdA, LdB, LdP, clrP, decB, data_in, clk);  
controller CON (LdA, LdB, LdP, clrP, decB, done, clk, eqz, start);
```

```
initial  
  begin  
    clk = 1'b0;  
    #3 start = 1'b1;  
    #500 $finish;  
  end  
  
always #5 clk = ~clk;
```

```
    initial  
      begin  
        #17 data_in = 17;  
        #10 data_in = 5;  
      end  
    initial  
      begin  
        $monitor ($time, " %d %b", DP.Y, done);  
        $dumpfile ("mul.vcd"); $dumpvars (0, MUL_test);  
      end  
  
endmodule
```



```

module MUL_test;
  reg [15:0] data_in;
  reg clk, start;
  wire done;

```

```

  MUL_datapath DP (eqz, LdA, LdB, LdP, clrP, decB, data_in, clk);
  controller CON (LdA, LdB, LdP, clrP, decB, done, clk, eqz, start);

```

```

  initial
  begin
    clk = 1'b0;
    #3 start = 1'b1;
    #500 $finish;
  end

```

```

  always #5 clk = ~clk;

```

```

    initial
    begin
      #17 data_in = 17;
      #10 data_in = 5;
    end
    initial
    begin
      $monitor ($time, " %d %b", DP.Y, done);
      $dumpfile ("mul.vcd"); $dumpvars (0, MUL_test);
    end
  endmodule

```

## THE TEST BENCH


0	x	x
6	x	0
35	0	0
45	17	0
55	34	0
65	51	0
75	68	0
85	85	0
88	85	1

# A Better Style of Modeling Data/Control Path


- In the previous example, in the “*always*” block activated by clock edge, both state change as well as computation of the next state is performed.
- A better and recommended approach:
  - Only trigger the state change in the clock activated “*always*” block.
  - In a separate “*always*” block using blocking assignments, compute the next state.
  - As in the previous example, in a separate “*always*” block, generate the control signals for the data path.

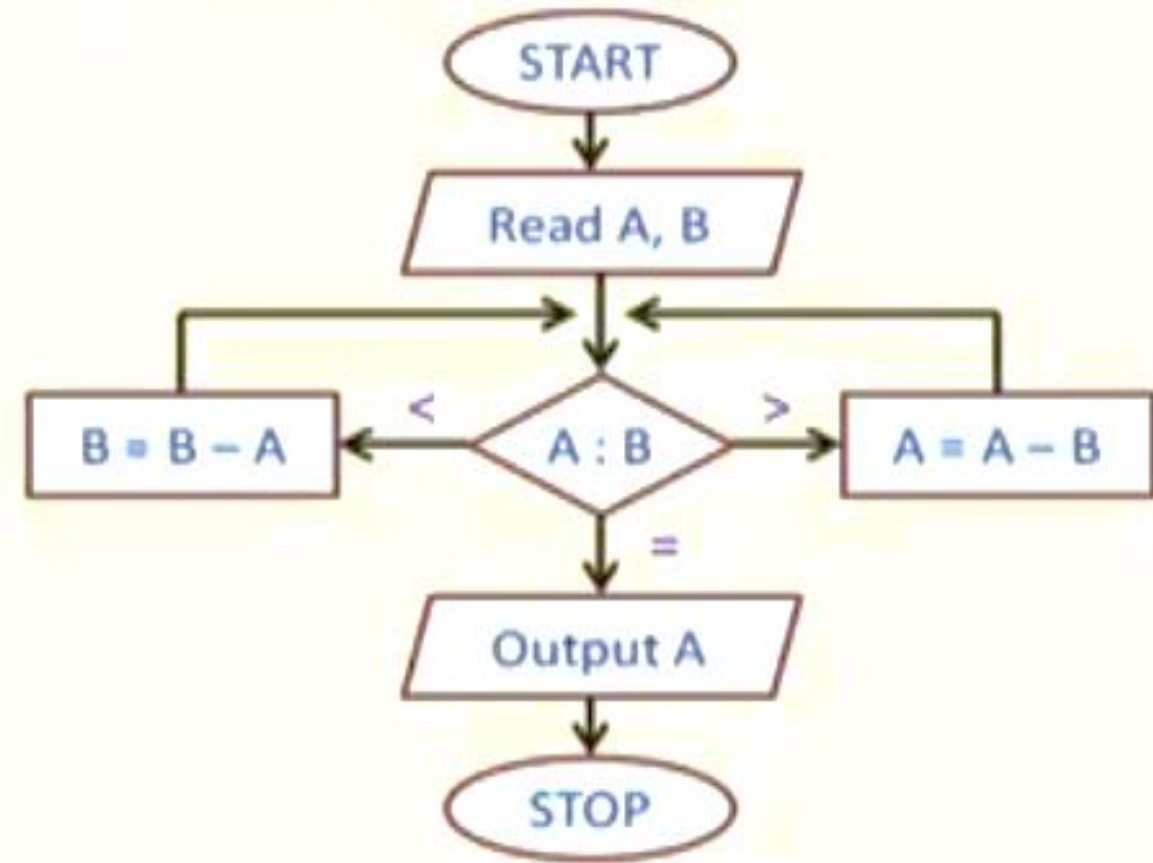
## Example 2: GCD Computation

- We consider a simple algorithm using repeated subtraction.
- We identify the functional blocks required in the data path, and the corresponding control signals.
- Then we design the FSM to implement the GCD computation algorithm using the data path.





## DATA PATH

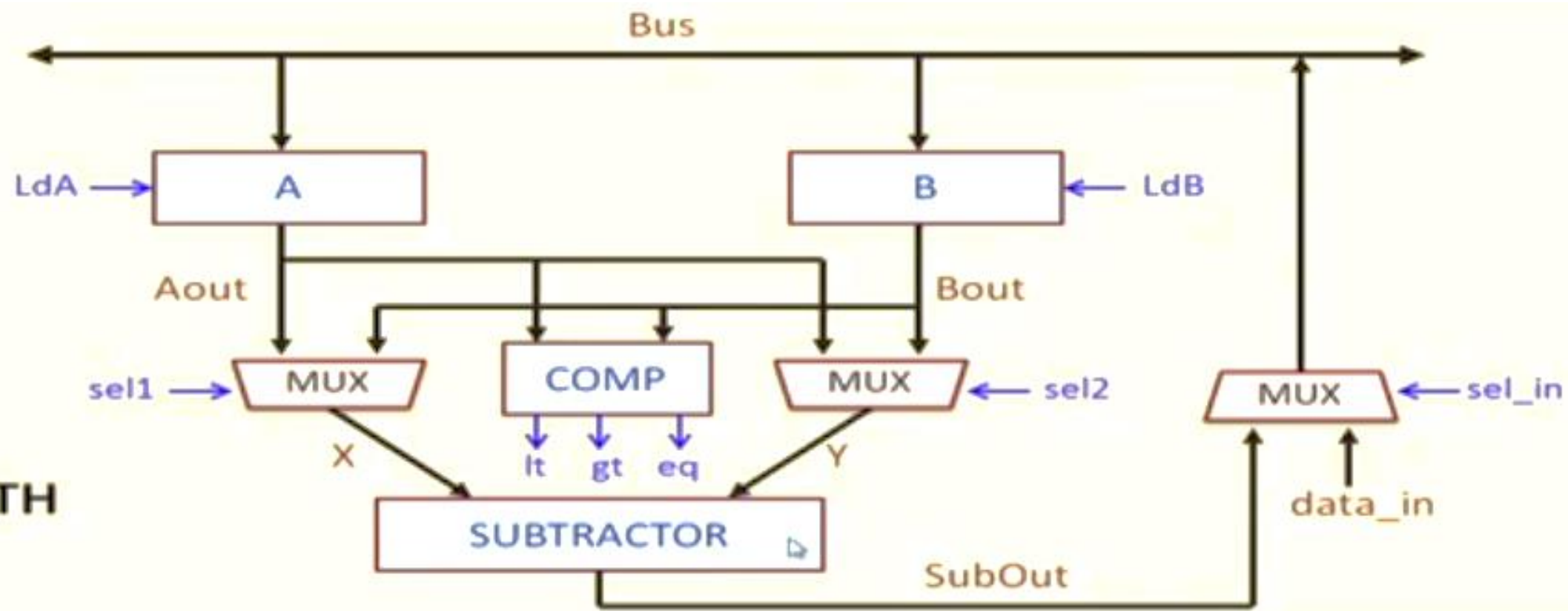

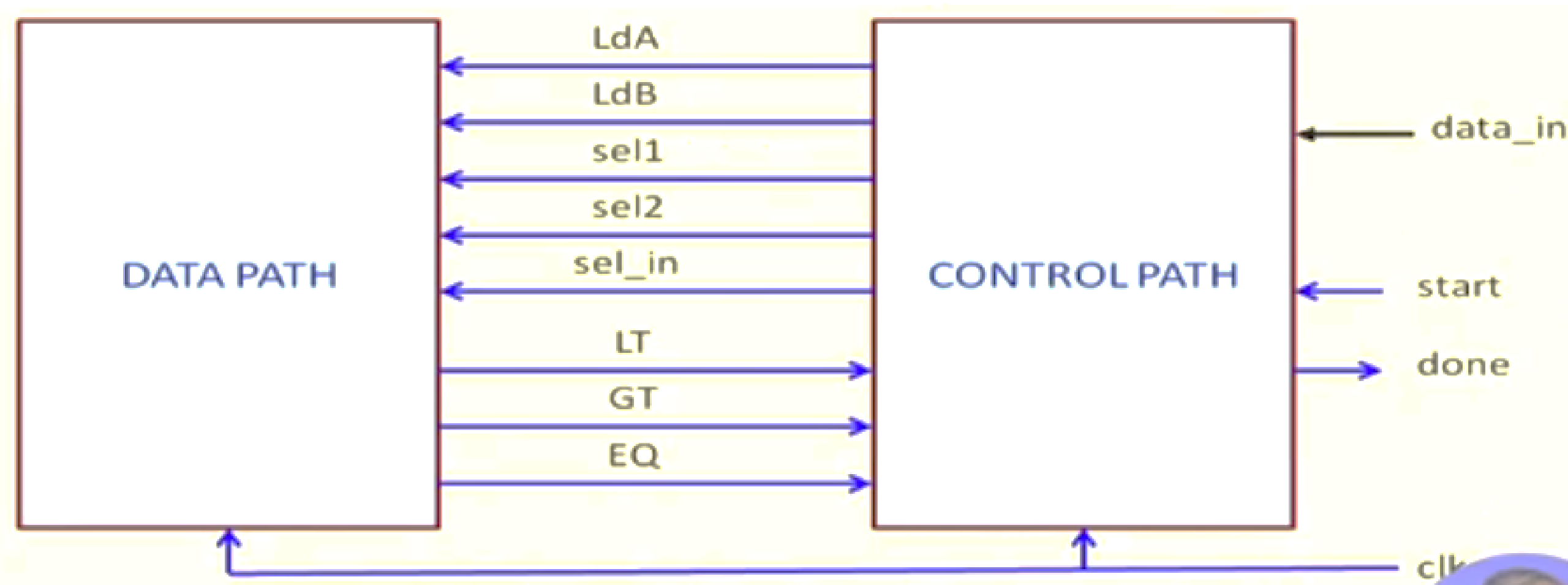



## CONTROL PATH

 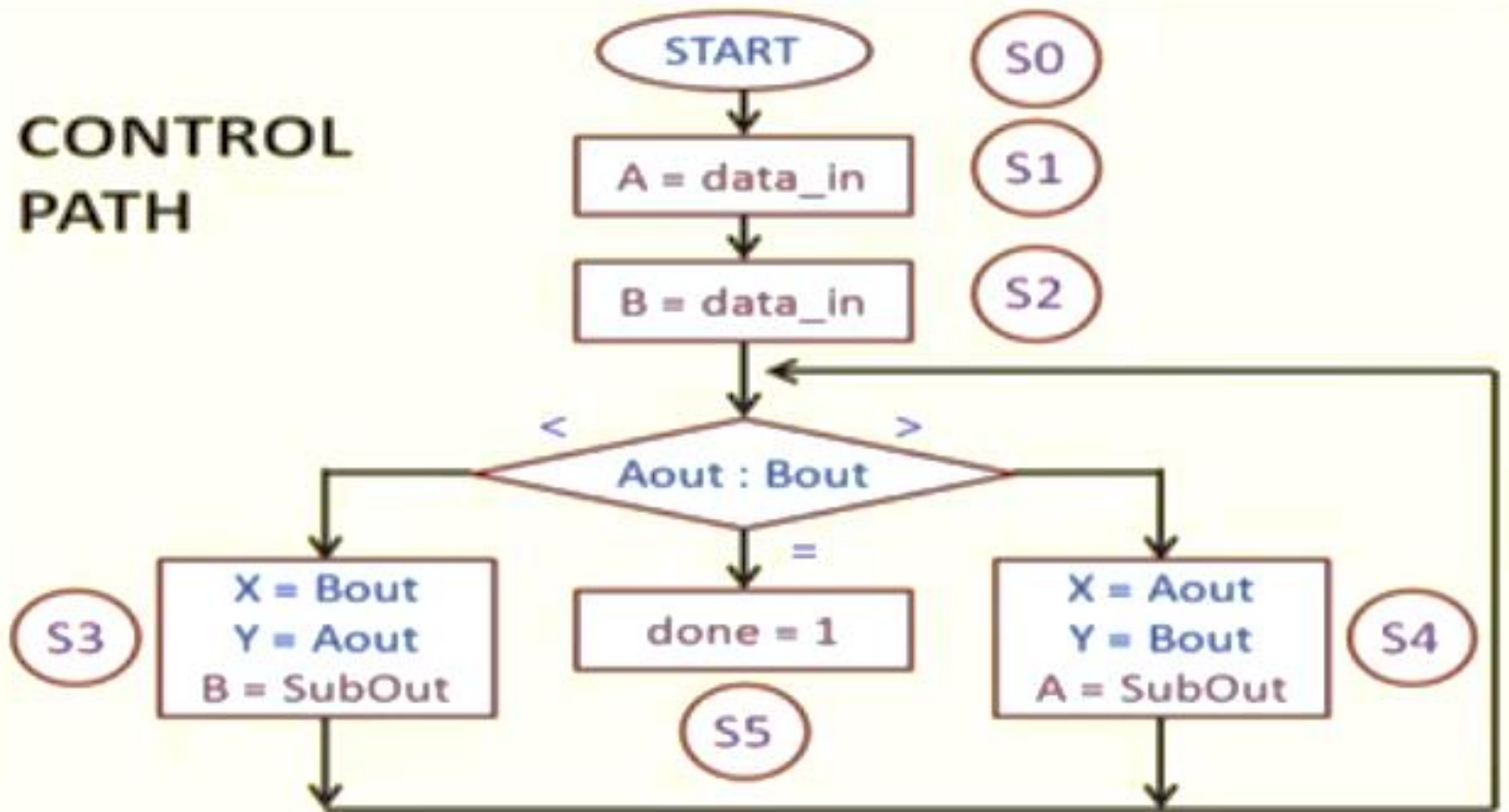



```
module GCD_datapath (gt, lt, eq, ldA, ldB, sel1, sel2, sel_in,
data_in, clk);
    input ldA, ldB, sel1, sel2, sel_in, clk;
    input [15:0] data_in;
    output gt, lt, eq;
    wire [15:0] Aout, Bout, X, Y, Bus, SubOut;

    PIPO A (Aout, Bus, ldA, clk);
    PIPO B (Bout, Bus, ldB, clk);
    MUX MUX_in1 (X, Aout, Bout, sel1);
    MUX MUX_in2 (Y, Aout, Bout, sel2);
    MUX MUX_load (Bus, SubOut, data_in, sel_in);
    SUB SB (SubOut, X, Y);
    COMPARE COMP (lt, gt, eq, Aout, Bout);
endmodule
```

**THE DATA  
PATH**

```

module FIFO (data_out, data_in,
              load, clk);
    input [15:0] data_in;
    input load, clk;
    output reg [15:0] data_out;
    always @(posedge clk)
        if (load) data_out <= data_in;
endmodule

```

```

module SUB (out, in1, in2);
    input [15:0] in1, in2;
    output reg [15:0] out;
    always @(*)
        out = in1 - in2;
endmodule

```

```

module COMPARE (lt, gt, eq, data1,
                data2);
    input [15:0] data1, data2;
    output lt, gt, eq;
    assign lt = data1 < data2;
    assign gt = data1 > data2;
    assign eq = data1 == data2;
endmodule

```

```

module MUX (out, in0, in1, sel);
    input [15:0] in0, in1;
    input sel;
    output [15:0] out;
    assign out = sel ? in1 : in0;
endmodule

```

```

module controller (ldA, ldB, sel1, sel2, sel_in, done, clk, lt, gt, eq, start);
  input clk, lt, gt, eq, start;
  output reg ldA, ldB, sel1, sel2, sel_in, done;

  reg [2:0] state;
  parameter S0=3'b000, S1=3'b001, S2=3'b010, S3=3'b011, S4=3'b100, S5=3'b101;

  always @(posedge clk)
    begin
      case (state)
        S0:    if (start) state <= S1;
        S1:    state <= S2;
        S2:    #2 if (eq) state <= S5;
              else if (lt) state <= S3;
              else if (gt) state <= S4;
        S3:    #2 if (eq) state <= S5;
              else if (lt) state <= S3;
              else if (gt) state <= S4;
        S4:    #2 if (eq) state <= S5;
              else if (lt) state <= S3;
              else if (gt) state <= S4;
        S5:    state <= S5;
        default: state <= S0;
      endcase
    end
end

```

**THE CONTROL  
PATH**

```

always @(state)
begin
case (state)
S0:    begin sel_in = 1;  ldA = 1;  ldB = 0; done = 0; end
S1:    begin sel_in = 1;  ldA = 0;  ldB = 1; end
S2:    if (eq) done = 1;
        else if (lt) begin
            sel1 = 1; sel2 = 0; sel_in = 0;
            #1 ldA = 0; ldB = 1;
        end
        else if (gt) begin
            sel1 = 0; sel2 = 1; sel_in = 0;
            #1 ldA = 1; ldB = 0;
        end
S3:    if (eq) done = 1;
        else if (lt) begin
            sel1 = 1; sel2 = 0; sel_in = 0;
            #1 ldA = 0; ldB = 1;
        end
        else if (gt) begin
            sel1 = 0; sel2 = 1; sel_in = 0;
            #1 ldA = 1; ldB = 0;
        end
end
end

```



```

S4:    if (eq) done = 1;
        else if (lt) begin
            sel1 = 1; sel2 = 0; sel_in = 0;
            #1 ldA = 0; ldB = 1;
        end
        else if (gt) begin
            sel1 = 0; sel2 = 1; sel_in = 0;
            #1 ldA = 1; ldB = 0;
        end

S5:    begin
        done = 1; sel1 = 0; sel2 = 0; ldA = 0;
        ldB = 0;
    end
    default: begin ldA = 0; ldB = 0; end
endcase
end

endmodule

```

## THE TEST BENCH

```
module GCD_test;
  reg [15:0] data_in;
  reg clk, start;
  wire done;

  reg [15:0] A, B;

  GCD_datapath DP (gt, lt, eq, ldA, ldB, sel1, sel2, sel_in, data_in, clk);
  controller CON (ldA, ldB, sel1, sel2, sel_in, done, clk, lt, gt, eq, start);

  initial
    begin
      clk = 1'b0;
      #3 start = 1'b1;
      #1000 $finish;
    end

  always #5 clk = ~clk;

  initial
    begin
      #12 data_in = 143;
      #10 data_in = 78;
    end

  initial
    begin
      $monitor ($time, " %d %b", DP.Aout, done);
      $dumpfile ("gcd.vcd"); $dumpvars (0, GCD_test);
    end

endmodule
```



## THE TEST BENCH

```

module GCD_test;
  reg [15:0] data_in;
  reg clk, start;
  wire done;

  reg [15:0] A, B;

  GCD_datapath DP (gt, lt, eq, ldA, ldB, sel1, sel2, sel_in, data_in, clk);
  controller CON (ldA, ldB, sel1, sel2, sel_in, done, clk, lt, gt, eq, start);

  initial
    begin
      clk = 1'b0;
      #3 start = 1'b1;
      #1000 $finish;
    end

  always #5 clk = ~clk;
initial
  begin
    #12 data_in = 143;
    #10 data_in = 78;
  end

  initial
    begin
      $monitor ($time, " %d %b", DP.Aout, done);
      $dumpfile ("gcd.vcd"); $dumpvars (0, GCD_test);
    end

endmodule

```

0	x	x
5	x	0
15	143	0
35	65	0
55	52	0
65	39	0
75	26	0
85	13	0
87	13	1

# **MODELING THE CONTROL PATH USING THE ALTERNATE APPROACH**

```
module controller (ldA, ldB, sel1, sel2, sel_in, done, clk, lt, gt, eq, start);  
  input clk, lt, gt, eq, start;  
  output reg ldA, ldB, sel1, sel2, sel_in, done;  
  reg [2:0] state, next_state;  
  parameter S0=3'b000, S1=3'b001, S2=3'b010, S3=3'b011, S4=3'b100, S5=3'b101;  
  always @(posedge clk)  
  begin  
    state <= next_state;  
  end
```

**THE CONTROL  
PATH**

```
always @(state)
begin
case (state)
S0:    begin sel_in = 1;  ldA = 1;  ldB = 0; done = 0; end
S1:    begin sel_in = 1;  ldA = 0;  ldB = 1; end
S2:    if (eq) begin done = 1; next_state = S5; end
        else if (lt) begin
            sel1 = 1; sel2 = 0; sel_in = 0; next_state = S3;
            #1 ldA = 0; ldB = 1;
        end
        else if (gt) begin
            sel1 = 0; sel2 = 1; sel_in = 0; next_state = S4;
            #1 ldA = 1; ldB = 0;
        end
S3:    if (eq) begin done = 1; next_state = S5; end
        else if (lt) begin
            sel1 = 1; sel2 = 0; sel_in = 0; next_state = S3;
            #1 ldA = 0; ldB = 1;
        end
        else if (gt) begin
            sel1 = 0; sel2 = 1; sel_in = 0; next_state = S4;
            #1 ldA = 1; ldB = 0;
        end
end
end
```

```

S4:    if (eq) begin done = 1; next_state = S5; end
        else if (lt) begin
            sell = 1; sel2 = 0; sel_in = 0; next_state = S3;
            #1 ldA = 0; ldB = 1;
        end
        else if (gt) begin
            sell = 0; sel2 = 1; sel_in = 0; next_state = S4;
            #1 ldA = 1; ldB = 0;
        end

S5:    begin
        done = 1; sell = 0; sel2 = 0; ldA = 0;
        ldB = 0; next_state = S5;
    end
    default: begin ldA = 0; ldB = 0; next_state = S0; end
endcase
end

endmodule

```




## Example 3: Booth's Multiplication

- In the conventional shift-and-add multiplication, for  $n$ -bit multiplication, we iterate  $n$  times.
  - Add either 0 or the multiplicand to the  $2n$ -bit partial product (depending on the next bit of the multiplier).
  - Shift the  $2n$ -bit partial product to the right.
- Essentially we need  $n$  *additions and  $n$  shift operations*.
- Booth's algorithm is an improvement whereby we can avoid the additions whenever consecutive 0's or 1's are detected in the multiplier.
  - Makes the process faster.


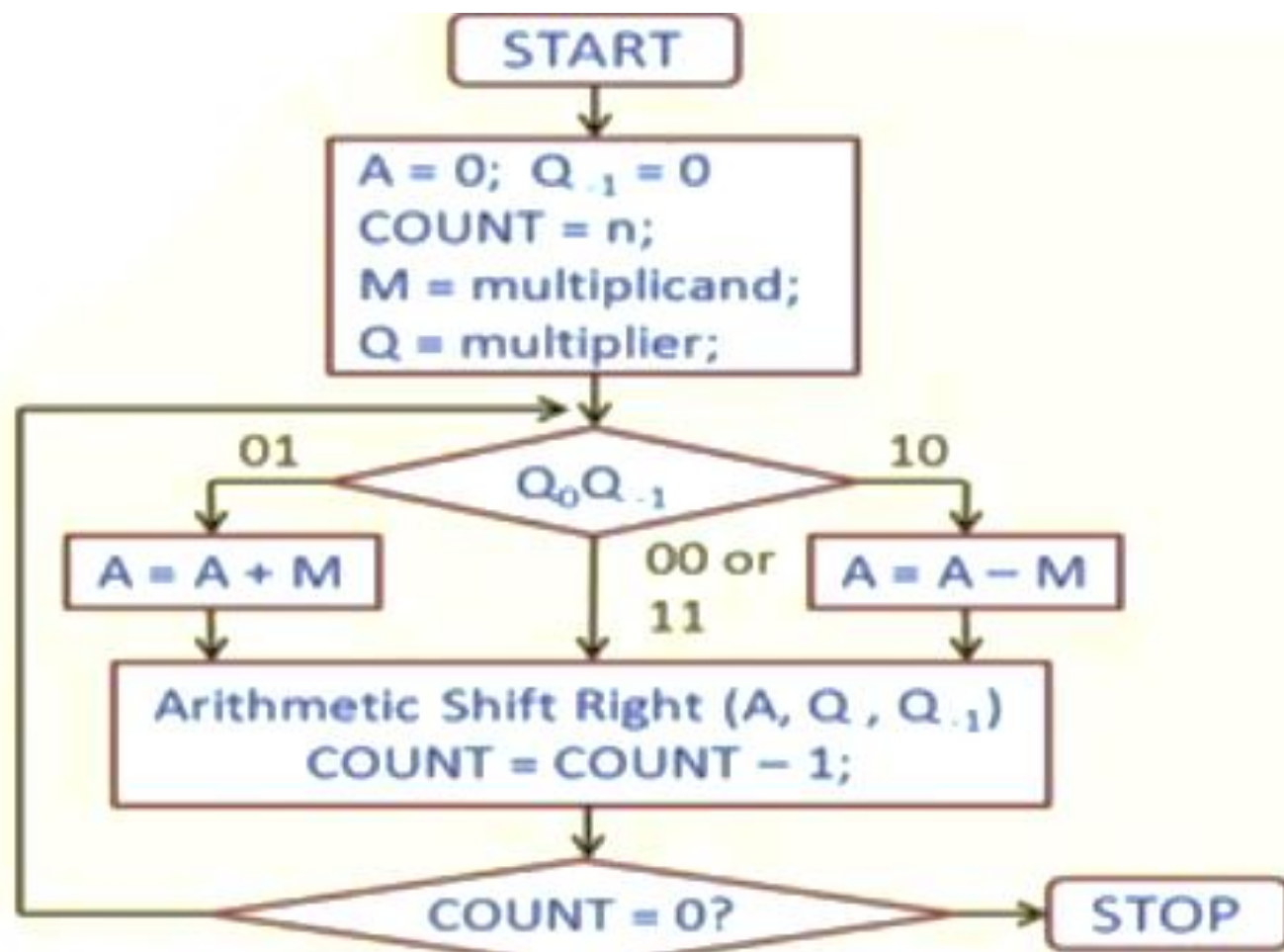
## Basic Idea Behind Booth's Algorithm

- We inspect two bits of the multiplier ( $Q_i, Q_{i-1}$ ) at a time.
  - If the bits are same (00 or 11), we only shift the partial product.
  - If the bits are 01, we do an addition and then shift.
  - If the bits are 10, we do a subtraction and then shift.
- $Q_{-1}$  is assumed to be equal to 0.
- Significantly reduces the number of additions / subtractions.



$M$ :  $n$ -bit multiplicand

$Q$ :  $n$ -bit multiplier

$A$ :  $n$ -bit temporary register

$Q_{-1}$ : 1-bit flip-flop

**Example 1:**  $(-10) \times (13)$

Assume 5-bit numbers.

M:  $(10110)_2$

-M:  $(01010)_2$

Q:  $(01101)_2$

Product = -130

$= (110111110)_2$

A	Q	Q <sub>-1</sub>		
0 0 0 0 0	0 1 1 0	1 0	Initialization	
0 1 0 1 0	0 1 1 0	1 0	A = A - M	Step 1
0 0 1 0 1	0 0 1 1	0 1	Shift	
1 1 0 1 1	0 0 1 1	0 1	A = A + M	Step 2
1 1 1 0 1	1 0 0 1	1 0	Shift	
0 0 1 1 1	1 0 0 1	1 0	A = A - M	Step 3
0 0 0 1 1	1 1 0 0	1 1	Shift	
0 0 0 0 1	1 1 1 1	0 1	Shift	Step 4
1 0 1 1 1	1 1 1 0 0	1	A = A + M	Step 5
1 1 0 1 1	1 1 1 1 0	0	Shift	

### Example 2:

$$(-31) \times (28)$$

Assume 6-bit numbers.

$$M: (100001)_2$$

$$-M: (011111)_2$$

$$Q: (011100)_2$$

$$\text{Product} = -868$$

$$= (110010 \\ 011100)_2$$

A	Q	Q <sub>-1</sub>
0 0 0 0 0 0	0 1 1 1 0	0 0
0 0 0 0 0 0	0 0 1 1 1	0 0
0 0 0 0 0 0	0 0 0 1 1	1 0
0 1 1 1 1 1	0 0 0 1 1	1 0
0 0 1 1 1 1	1 0 0 0 1	1 1
0 0 0 1 1 1	1 1 0 0 0	1 1
0 0 0 0 1 1	1 1 1 0 0	0 1
1 0 0 1 0 0	1 1 1 0 0 0	1
1 1 0 0 1 0	0 1 1 1 0 0	0

Initialization

Shift Step 1

Shift Step 2

$A = A - M$  Step 3

Shift


Shift Step 4

Shift Step 5


$A = A + M$  Step 6

Shift




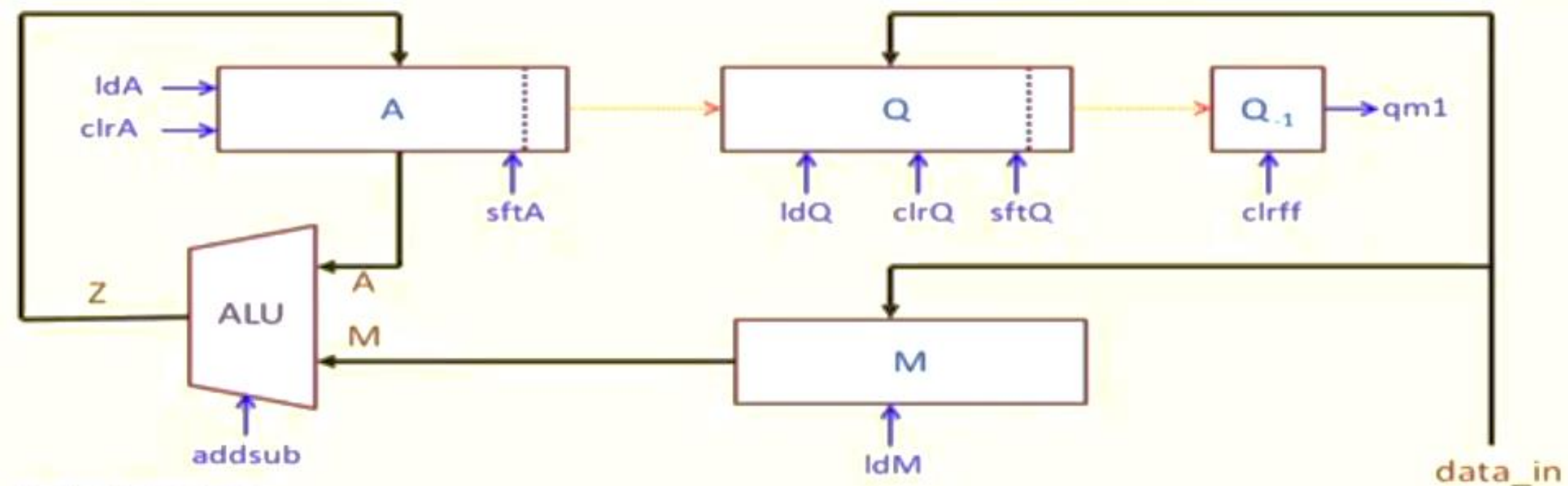


**DATA PATH**

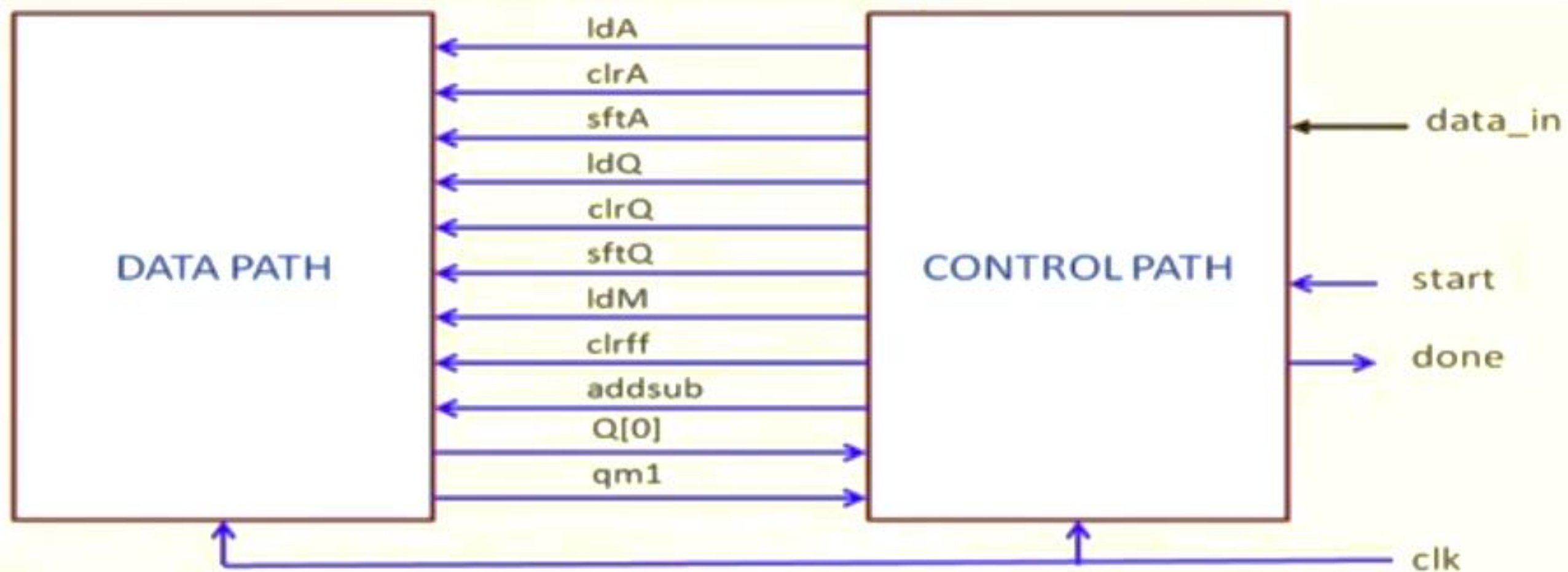



# CONTROL PATH

 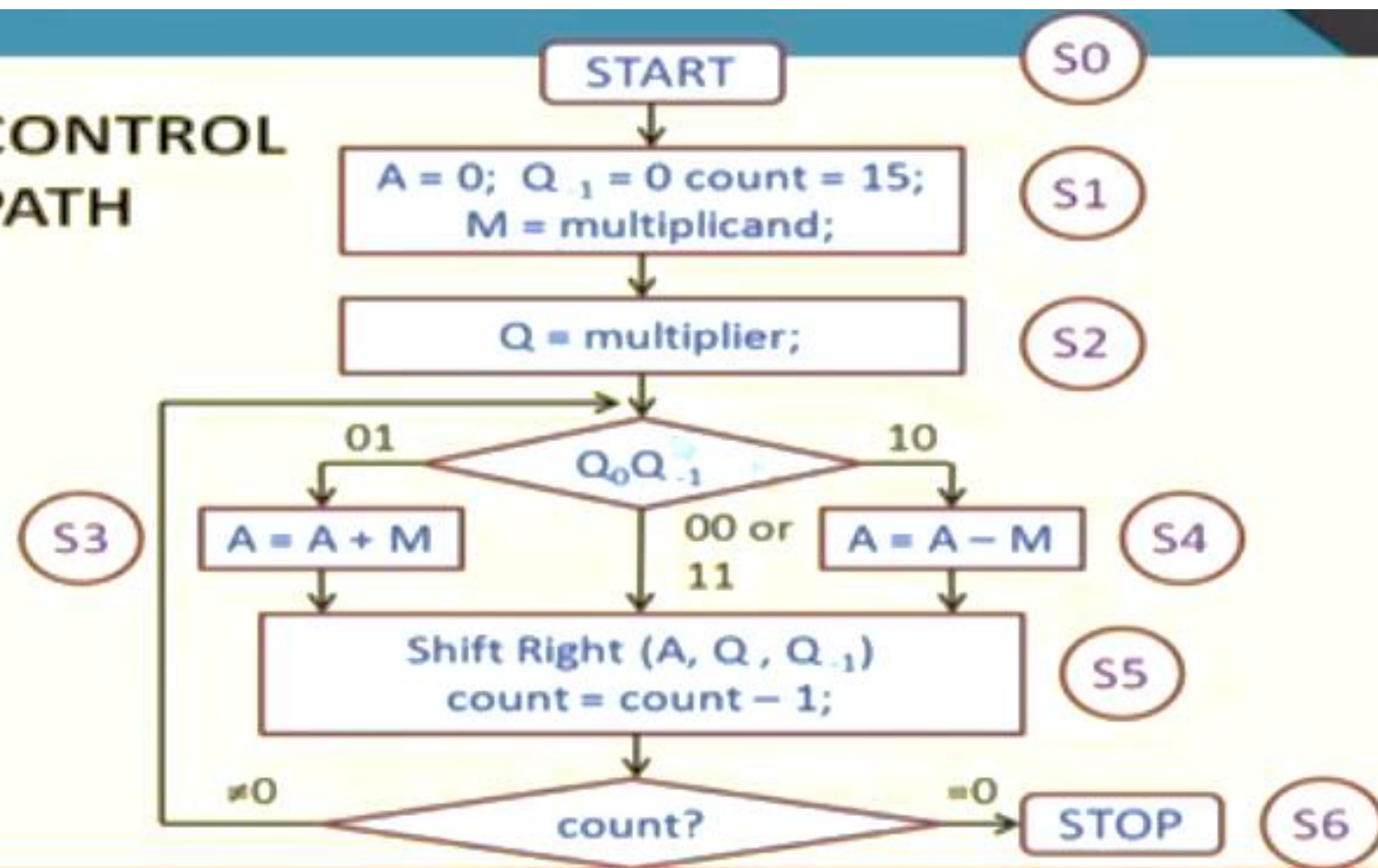

```

module BOOTH (ldA, ldQ, ldM, clrA, clrQ, clrff, sftA, sftQ,
              addsub, decr, ldcnt, data_in, clk, qm1, eqz);

  input ldA, ldQ, ldM, clrA, clrQ, clrff, sftA, sftQ, addsub, clk;
  input [15:0] data_in;
  output qm1, eqz;
  wire [15:0] A, M, Q, Z;
  wire [4:0] count;

  assign eqz = ~&count;

  shiftreg AR (A, Z, A[15], clk, ldA, clrA, sftA);
  shiftreg QR (Q, data_in, A[0], clk, ldQ, clrQ, sftQ);
  dff QM1 (Q[0], qm1, clk, clrff);
  PIPO MR (data_in, M, clk, ldM);
  ALU AS (Z, A, M, addsub);
  counter CN (count, decr, ldcnt, clk);
endmodule

```

**THE DATA  
PATH**

```

module shiftreg (data_out,data_in,
                 s_in, clk, ld, clr, sft);
    input s_in, clk, ld, clr, sft;
    input [15:0] data_in;
    output reg [15:0] data_out;

    always @(posedge clk)
        begin
            if (clr) data_out <= 0;
            else if (ld)
                data_out <= data_in;
            else if (sft)
                data_out <= {s_in,data_out[15:1]};
        end
endmodule

```

```

module PIFO (data_out,data_in, clk, load);
    input [15:0] data_in;
    input load, clk;
    output reg [15:0] data_out;

    always @(posedge clk)
        if (load) data_out <= data_in;
endmodule

module dff (d, q, clk, clr);
    input d, clk, clr;
    output reg q;

    always @(posedge clk)
        if (clr) q <= 0;
        else q <= d;
endmodule

```

```
module ALU (out, in1, in2, addsub);  
  input [15:0] in1, in2;  
  input addsub;  
  output reg [15:0] out;  
  
  always @(*)  
  begin  
    if (addsub == 0) out = in1 - in2;  
    else out = in1 + in2;  
  end  
endmodule
```

```
module counter (data_out, decr, ldcnt, clk)  
  input decr, clk;  
  output [4:0] data_out;  
  
  always @(posedge clk)  
  begin  
    if (ldcnt) data_out < 5'b10000;  
    else if (decr) data_out <= data_out - 1;  
  end  
endmodule
```



```

module controller (ldA, clrA, sftA, ldQ, clrQ, sftQ, ldM, clrff, addsub, start,
                  decr, ldcnt, done, clk, q0, qm1);
    input clk, q0, qm1, start;
    output reg ldA, clrA, sftA, ldQ, clrQ, sftQ, ldM, clrff, addsub, decr, ldcnt, done;
    reg [2:0] state;
    parameter S0=3'b000, S1=3'b001, S2=3'b010, S3=3'b011, S4=3'b100, S5=3'b101, S6=3'b110;
    always @(posedge clk)
        begin
            case (state)
                S0:    if (start) state <= S1;
                S1:    state <= S2;
                S2:    #2 if ({q0,qm1}==2'b01) state <= S3;
                     else if ({q0,qm1}==1'b10) state <= S4;
                     else state <= S5;
                S3:    state <= S5;
                S4:    state <= S5;
                S5:    #2 if (((q0,qm1)==2'b01) && !eqz) state <= S3;
                     else if (((q0,qm1)==2'b10) && !eqz) state <= S4;
                     else if (eqz) state <= S6;
                S6:    state <= S6;
                default: state <= S0;
            endcase
        end
end

```

**THE CONTROL  
PATH**



```

always @(state)
begin
    case (state)
        S0:    begin clrA = 0; ldA = 0; sftA = 0; clrQ = 0; ldQ = 0; sftQ = 0;
                ldM = 0; clrff = 0; done = 0; end
        S1:    begin clrA = 1;  clrff = 1;  ldcnt = 1; ldM = 1; end
        S2:    begin clrA = 0; clrff = 0; ldcnt = 0; ldM = 0; ldQ = 1; end
        S3:    begin ldA = 1; addsub = 1; ldQ = 0; sftA = 0; sftQ = 0; decr = 0; end
        S4:    begin ldA = 1; addsub = 0; ldQ = 0; sftA = 0; sftQ = 0; decr = 0; end
        S5:    begin sftA = 1; sftQ = 1; ldA = 0; ldQ = 0; decr = 1; end
        S6:    done = 1;
        default: begin clrA = 0; sftA = 0; ldQ = 0; sftQ = 0; end
    endcase
end

```

- Test bench can be written similarly.
- Points to note:
  - The timing must be very clearly analyzed and signals activated at proper time instances in the test bench.
  - Otherwise, the simulation results will not come correct, though the module descriptions may be fine.